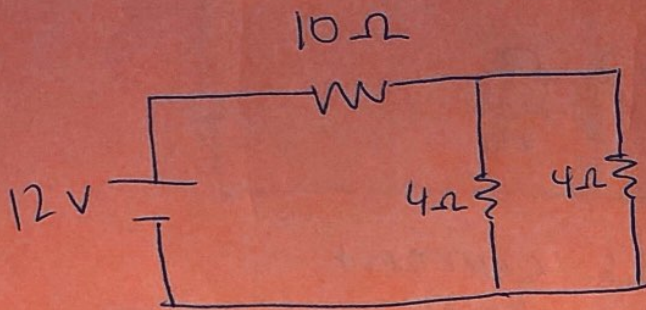


## Combination Circuits :

### Rules

In a loop : Voltage in equals voltage out.

At a junction : current in equals current out.



$10\ \Omega$  is in Series

$4\ \Omega + 4\ \Omega$  are in parallel

Step 1 : solve for the equivalent resistance of the parallel circuit

"collapse the parallel circuit"

$$\frac{1}{R_E} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R_E} = \frac{1}{4} + \frac{1}{4}$$

$$\frac{1}{R_E} = .5$$

$$R_E = \frac{1}{.5}$$


$$R_E = 2\ \Omega$$

Step 2: Redraw circuit

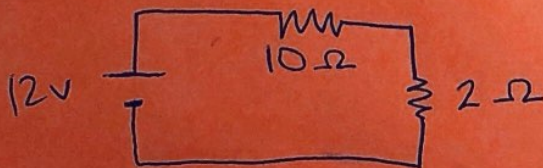



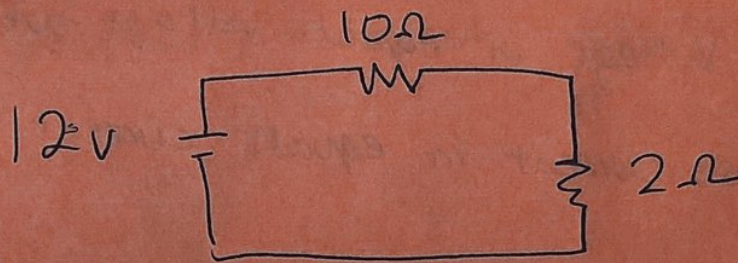Step 3: solve for total resistance (series)



$$R_T = 10\Omega + 2\Omega$$

$$R_T = 12\Omega$$

Step 4: Solve for total current

$$V = IR$$

$$\frac{12V}{12} = \frac{I(12\Omega)}{12}$$

$$1A = I$$

Step 5: solve for voltage drop at each resistor

At  $10\Omega$  resistor

$$V = IR$$

$$V = (1A)(10\Omega)$$

$$V = 10V$$

At  $2\Omega$  resistor


$$V = IR$$

$$V = (1A)(2\Omega)$$

$$V = 2V$$



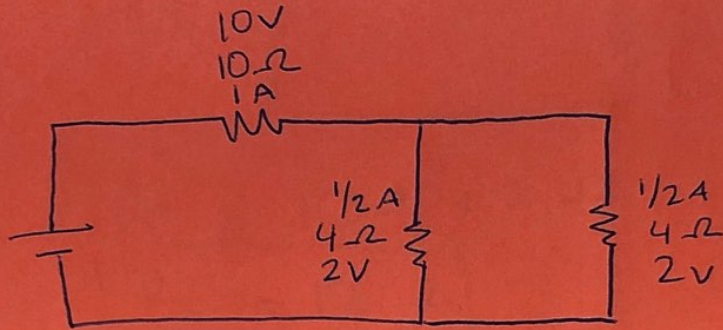Step 6: Go back to original circuit and solve for current and voltage at each resistor.



\* Remember that current is constant in a series circuit and voltage is constant in a parallel circuit.

Series  $I = \text{current}$

Parallel  
voltage