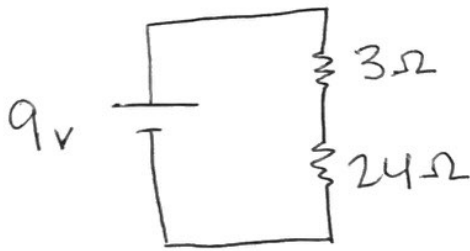


Series circuit: only one pathway

Series \rightarrow I is current - current is constant in Series.



① Find total resistance:

$$R_T = R_1 + R_2 \dots$$

$$R_T = 3\Omega + 24\Omega$$

$$R_T = 27\Omega$$

② Find total current:

$$V = IR$$

$$9V = I (27\Omega)$$

$$\frac{1}{3}A = I$$

$$.33A = I$$

③ Find voltage drop at each resistor:

$$R_1 = V = IR$$

$$V = (.33)(3\Omega)$$

$$V = 1V$$

$$R_2 = V = IR$$

$$V = (.33)(24\Omega)$$

$$V = 8V$$

Parallel:



Voltage remains constant in parallel circuits

at $18\Omega \rightarrow 9V$

at $3\Omega \rightarrow 9V$

Solve for current: at each resistor:

$$I = \frac{V}{R} \quad I = \frac{9V}{18\Omega} = 0.5A$$

$$I = \frac{V}{R} \quad I = \frac{9V}{3\Omega} = 3A$$

Total current 3.5A

2 rules:

① Junction rule:

Where the Amps meet at a junction \rightarrow add them together.

Where the amps leave the junction \rightarrow subtract them.

$$I_{in} = I_{out}$$




② in a loop: Voltage in = Voltage out.

Parallel Circuits: more than one pathway.


Each loop is basically it's own circuit.

Parallel

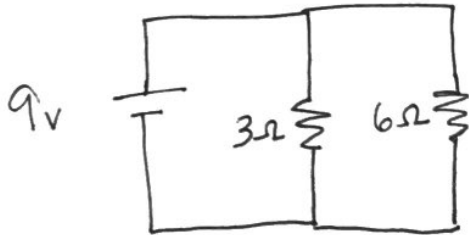↓
-v- is voltage - voltage is constant in parallel



This circuit has multiple pathways.

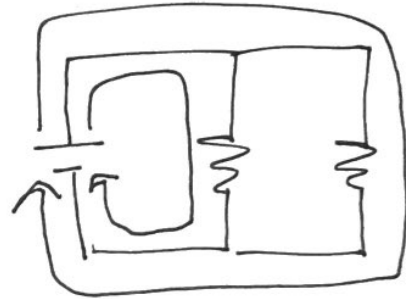

To find the current in each pathway:

$$V = IR$$

$$9V = I(3\Omega)$$

$$\frac{9}{3} = \frac{I}{3}$$

$$3A = I$$

$$V = IR$$

$$9V = I(6\Omega)$$

$$\frac{9}{6} = \frac{I}{6}$$

$$1.5A = I$$

Power: determines how "powerful" object is.

- how bright the lightbulb is
- how strong your hair dryer is
- how fast the fan turns.

$$P = IV$$

P = power (watts)

I = current (amps)

V = voltage (volts)