

Study Guide

Coulomb's Law

$$F_e = \frac{k q_1 q_2}{d^2}$$

F_e = electrostatic force (N)

$k = 9 \times 10^9$ ← always!

q_1 = charge of 1st particle (C)

q_2 = charge of 2nd particle (C)

d = distance (m)

★ opposites attract - when the charges have a negative charge and a positive, they attract.

★ Like charges repel - when charges have positive + positive - repel
negative + negative - repel

Inverse square Law

$$F_e = \frac{k q_1 q_2}{d^2}$$

On the top of the formula:
When you double the charge,
it doubles the force.

Ex:

$$\frac{1}{4} F_e = \frac{k q_1 q_2}{2d^2}$$

$2^2 = 4$

On the bottom of the formula:
When you double the distance,
because it is squared, and on
bottom, it is $1/4$ th the force.

Ohm's Law

$$V = IR$$

V = Voltage (V)

I = current (A)


R = Resistance (Ω)

Voltage is the "battery", current travels through the "wire", resistor is the "light bulb" in a circuit

Voltage drop = potential difference.

Series circuit

- current remains constant
- one path

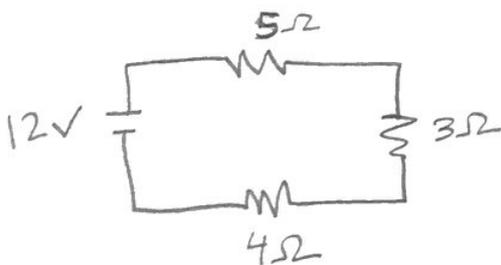

To find Total resistance:

$$R_T = R_1 + R_2 + R_3 \dots$$

$$5 + 3 + 4 = 12 \Omega$$

Use total voltage & total resistance to find current.

$$V = IR$$


$$12V = (I)(12\Omega)$$

$$\frac{12}{12} = \frac{I}{12}$$

$$1A = I$$

Parallel circuit

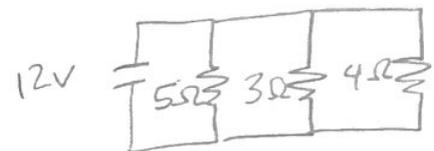- voltage remains constant
- multiple paths



To find total resistance:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{3} + \frac{1}{4}$$

$$R_T = 1.3 \Omega$$

To find current at each resistor: (voltage stays constant)

$$V = IR$$

$$12V = I(5)$$

$$\frac{12}{5} = 2.4A$$


$$12V = I(3)$$

$$\frac{12}{3} = 4A$$

$$12V = I(4)$$

$$\frac{12}{4} = 3A$$

Combination Circuit:

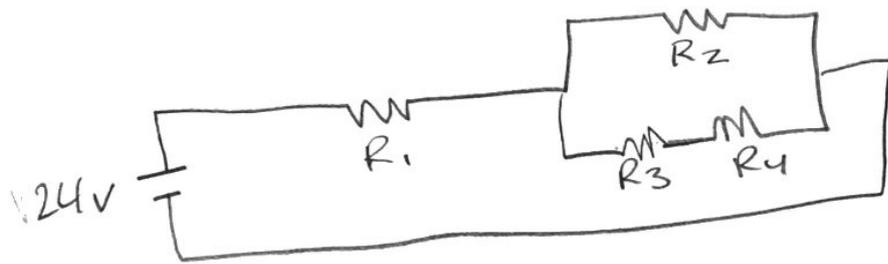

R_1 is in series

R_3 & R_4 are in series within the parallel

R_2 is in parallel

Collapse resistors to get them into a series.

Solve for total current

↓
constant in series

Use current to solve for voltage at resistors

↓
constant in parallel

Build the circuit back up to solve for current and voltage at each resistor.

Use $V=IR$ to solve for missing information.

Voltmeter - measures voltage

Ammeter - measures current

Fuses and circuit breakers are used to regulate.

Power

$$P = IV$$

P = power (watts)

I = current (A)

V = voltage (V)

Magnets

North and South pole

Opposites attract.

Magnetic field - more lines, stronger field.

Electromagnets:

Current running through wire.

Wrapping a wire into coils makes the magnetic field stronger → solenoid

Used to make a motor

Motors: electrical energy into kinetic energy

Generators: kinetic energy into electrical energy.