1. A negative charge of -4 x 10^{-7} C and a positive charge of 7 x 10^{-5} C are separated by 0.8 m. What is the force between the charges?

Formula: Plug in numbers: $(9 \times 10^{9})(-4 \times 10^{-7})(7 \times 10^{-5})$ $= \frac{4 \times 9 \cdot 92}{d^{2}}$ $= \frac{39}{10} \times 9 \times 10^{-1} \times 10^{-5} \times 10^{-5}$

2. A flashlight uses a standard 3 V battery. How much resistance is in the circuit if it uses a current of 0.04 A?

3. What current flows through a hair dryer plugged into a 123 Volt circuit if it has a resistance of 21 ohms?

Formula: Plug in numbers: $\frac{123v = (1)(2152)}{21}$ $\frac{5.86A}{21}$

4. A light bulb has a resistance of 15 ohms and a maximum current of 23 A. How much voltage can be applied before the bulb will break?


Formula:	Plug in numbers:	Answer with units:
V=IR	150 V=(23A)(15D)	345V

5. In a series circuit, a 9 V battery is connected to three resistors: 6 Ω . 13 Ω , and 20 Ω . What is the total resistance?

resistance? Formula:	Plug in numbers:	Answer with units:
RT = R1 + R2+R3	652 + 1352 + 2012	392
	i i	

6. In a parallel circuit, a 9 V battery is connected to three resistors: 4Ω , 13Ω and 27Ω . What is the total resistance?

Formula:	Plug in numbers:	Answer with units:
一个一个十一个	$\frac{1}{4} + \frac{1}{13} + \frac{1}{21}$	2.71

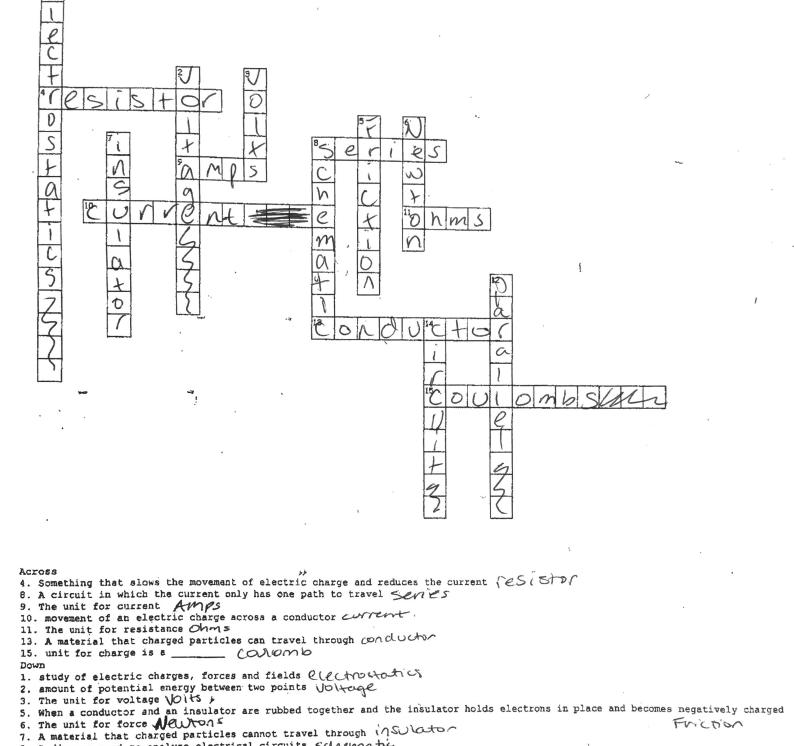

ds were placed into the puzzle

Created by Puzzlemaker at DiscoveryEducation.com





14. path in which a current is conducted Circuit

B. A diagram used to analyze electrical circuits Schematic

12. circuit in which a current has more than one path to take is a ____ circuit parallel